

FULL ADDER

CODE:

```
`timescale 1ns/1ps
module full(a,b,cin,s,cout);
input a,b,cin;
output s,cout;

assign s = a^b^cin;
assign cout = (a & b ) | (b & cin ) | (cin & a ) ;

endmodule
```

TEST BENCH:

```
timescale 1ns/1ps
module full_test;
reg a,b,cin;
wire s,cout;

full uut(a,b,cin,s,cout);

initial begin
a = 0; b = 0; cin = 0;
#10
a = 0; b = 0; cin = 1;
#10
a = 0; b = 1; cin = 0;
#10
a = 0; b = 1; cin = 1;
#10
a = 1; b = 0; cin = 0;
#10
a = 1; b = 0; cin = 1;
```


```

#10
a = 1; b = 1; cin = 0;
#10
a = 1; b = 1; cin = 1;
#10
$finish();
end

endmodule

```

OUTPUT:

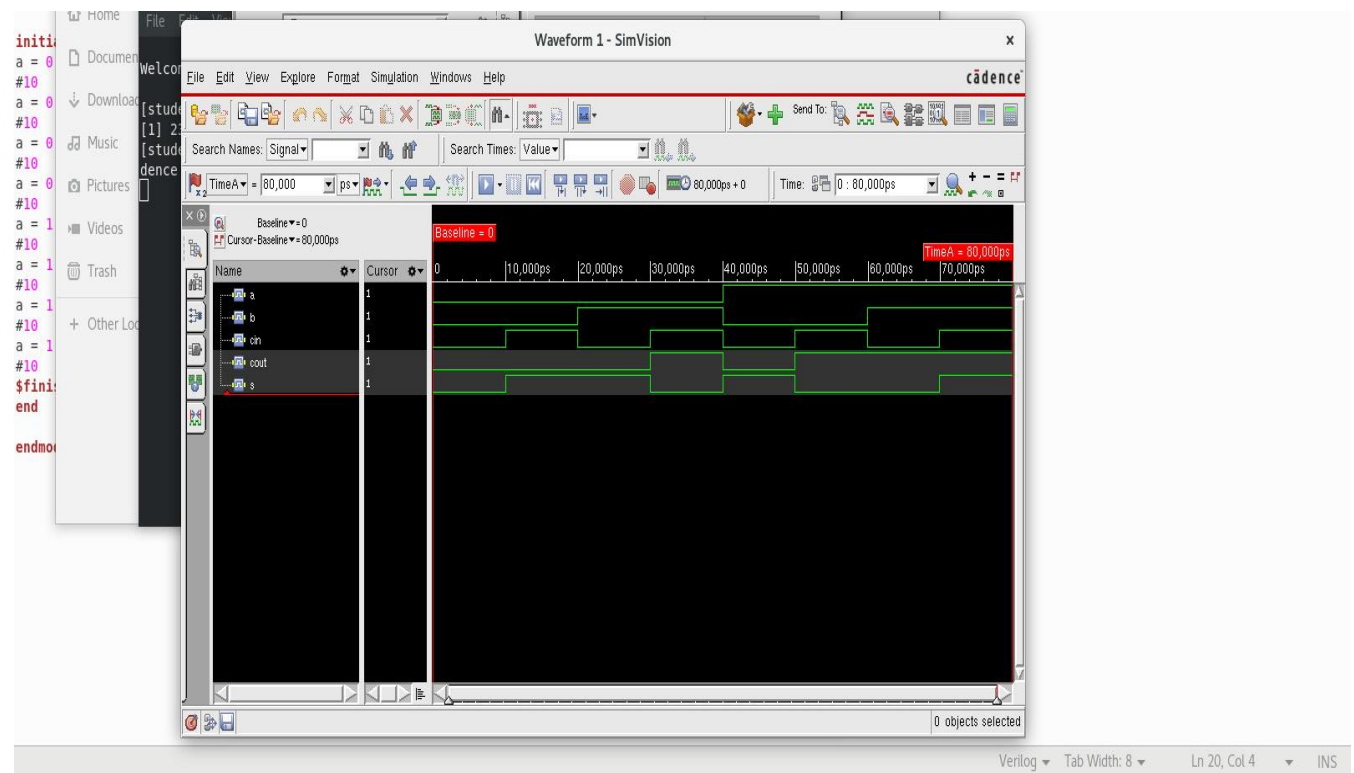

REFLECTION:

1. Understood how to add single bits (0 or 1) together, including the concept of a carry bit.
2. understood how full adders form the building block for more complex arithmetic circuits like multi-bit adders.

7 SEGMENT

CODE:

```
module segment7(bcd,seg);

    //Declare inputs,outputs and internal variables.
    input [3:0] bcd;
    output [6:0] seg;
    reg [6:0] seg;

    //always block for converting bcd digit into 7 segment format
    always @(bcd)
    begin
        case (bcd) //case statement
            0 : seg = 7'b0000001;
            1 : seg = 7'b1001111;
            2 : seg = 7'b0010010;
            3 : seg = 7'b0000110;
            4 : seg = 7'b1001100;
            5 : seg = 7'b0100100;
            6 : seg = 7'b0100000;
            7 : seg = 7'b0001111;
            8 : seg = 7'b0000000;
            9 : seg = 7'b0000100;
            //switch off 7 segment character when the bcd digit is not a decimal number.
            default : seg = 7'b1111111;
        endcase
    end

Endmodule
```

TEST BENCH:

```
module tb_segment7;
```

```

reg [3:0] bcd;
wire [6:0] seg;
integer i;


// Instantiate the Unit Under Test (UUT)
segment7 uut (
.bcd(bcd),
.seg(seg)
);

//Apply inputs
initial begin
for(i = 0;i < 16;i = i+1) //run loop for 0 to 15.
begin
bcd = i;
#10; //wait for 10 ns
end
end

endmodule

```

OUTPUT:

 

Reflection:

1. 7-segment display has practical applications in various embedded systems, such as digital clocks, temperature displays, and instrumentation panels, exposing students to real-world engineering challenges.

UP DOWN COUNTER

CODE:

```
`timescale 1ns/1ps
//Defining Module
module counter(clk,rst,m,count);
//Defining Inputs and Outputs (4bit)
input clk,rst,m;
output reg [3:0]count;
//The Block is executed when EITHER of positive edge of clock
//Both are independent events or Neg Edge of Rst arrives
always@(posedge clk or negedge rst)
begin
if(!rst)
count=0;
if(m)
count=count+1;
else
count=count-1;
end
Endmodule
```

TEST BENCH:


```
`timescale 1ns/1ps // Creating Time Scale as in Source Code
module counter_test; // Defining Module Name without Port List
reg clk, rst,m; // Defining I/P as Registers [to Hold Values]
```

```

wire [3:0] count; // Defining O/P as Wires [To Probe Waveforms]
initial
begin
clk=0; // Initializing Clock and Reset
rst=0;#25; // All O/P is 4'b0000 from t=0 to t=25ns.
rst=1; // Up-Down counting is allowed at posedge clk
end
initial
begin
m=1; // Condition for Up-Count
#600 m=0; // Condition for Down-Count
rst=0;#25;
rst=1;
#500 m=0;
end
counter counter1(clk,rst,m,count); // Instantiation of Source Code
always #5 clk=~clk; // Inverting Clk every 5ns
initial
#1400 $finish; // Finishing Simulation at t=1400ns
endmodule

```

OUTPUT:

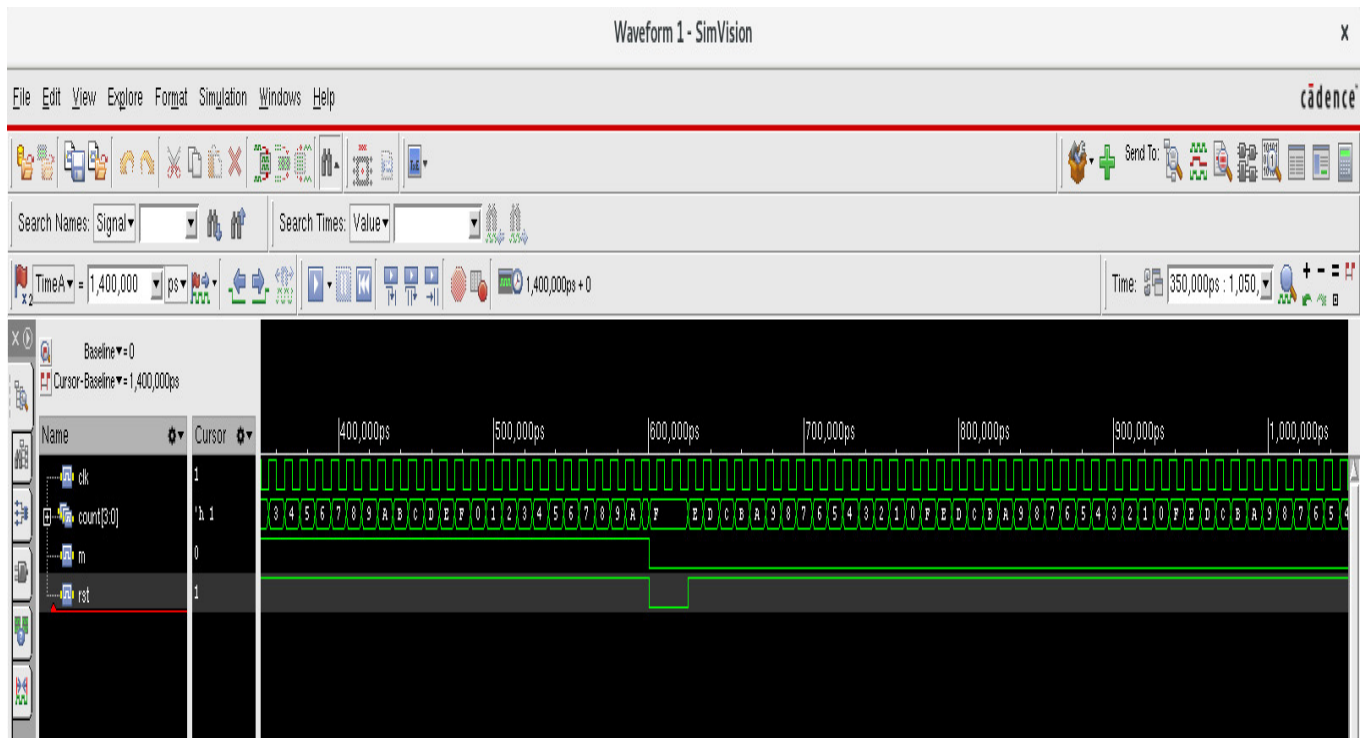

Reflection:

1. understanding of the process that transforms your written code into a program that your computer can understand and execute.
2. Learned how to create a visual representation of how data changes over time, helping you comprehend and analyze the behavior of programs or circuits that involve signals.

Class 3: 13 / 3 / 24

4 to 1 MUX

Code:

```
module multiplexer_4_to_1 ( output reg z, input [3:0] a, input sel );
  always @*
  case (sel)
    2'b00: z = a[0];
    2'b01: z = a[1];
    2'b10: z = a[2];
    2'b11: z = a[3];
  endcase
Endmodule
```

Test Bench:

```
`timescale 1ns/1ns
```


```
module multiplexer_4_to_1 (
  output reg z,
  input [3:0] a,
  input sel
);
```

```

always @*
  case (sel)
    2'b00: z = a[0];
    2'b01: z = a[1];
    2'b10: z = a[2];
    2'b11: z = a[3];
  endcase
Endmodule

```

Output:

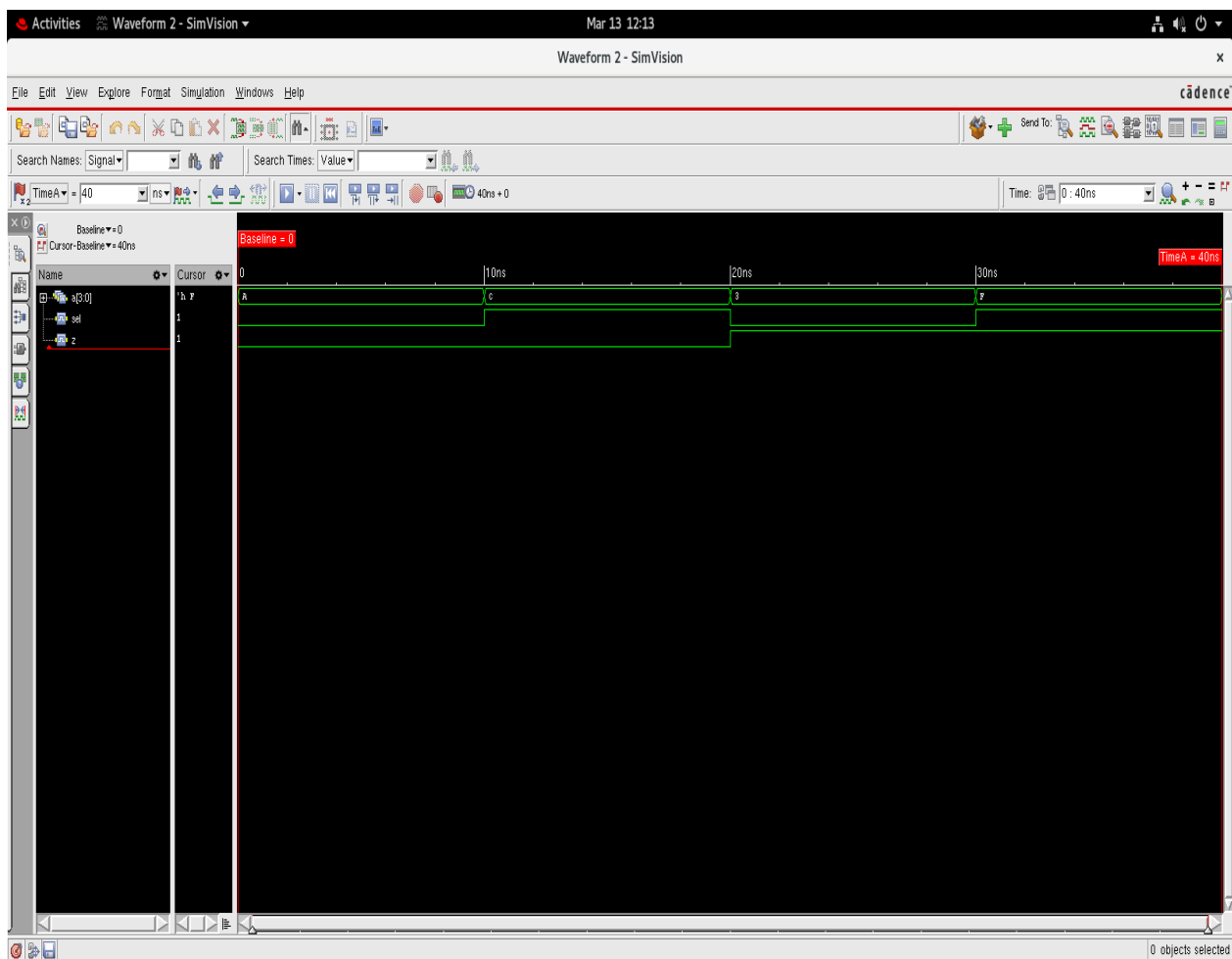

Reflection:

1. It is the best practice to explicitly specify whether a variable is a register or a wire..
2. The "reg" keyword is essential for declaring a variable as a register, signaling that it can hold values within procedural blocks such as "always" or "initial" blocks.

Class 4: 23 / 3 / 24

Half adder using pipeline

Code:

```
module half_adder (input a,b,output sum,carry);
assign sum = a ^ b;
assign carry = a & b;
endmodule
```

```
module full_adder2( input a,b,cin,clk, output sum,carry);
wire c1,c2,c3; reg pe1,pe2;
half_adder ha0(a,b,c1,c2);
half_adder ha1(pe1,cin,sum,c3);
assign carry = c3 | pe2 ;
always @(posedge clk)
begin
pe1=c1;
pe2=c2;
end
endmodule
```

Test bench:

```
module full_adder_Tb;

    reg a;
    reg b;
    reg cin;
    reg clk;
    wire sum;
    wire carry;
    full_adder uut (
        .a(a),
        .b(b),
        .cin(cin),
        .clk(clk),
        .sum(sum),
        .carry(carry)
    );
    always #5 clk = ~clk;


    initial begin
        a = 0;
        b = 0;
        cin = 0;
        clk = 0;
        #100;
        a = 1;
        b = 1;
        cin = 1;
        clk = 0;
        #100;
        a = 0;
        b = 1;
        cin = 0;
        clk = 0;
        #100;
        a = 1;
        b = 1;
        cin = 0;
        clk = 0;
```

```
#100;
```

```
end
```

```
endmodule
```

Output :

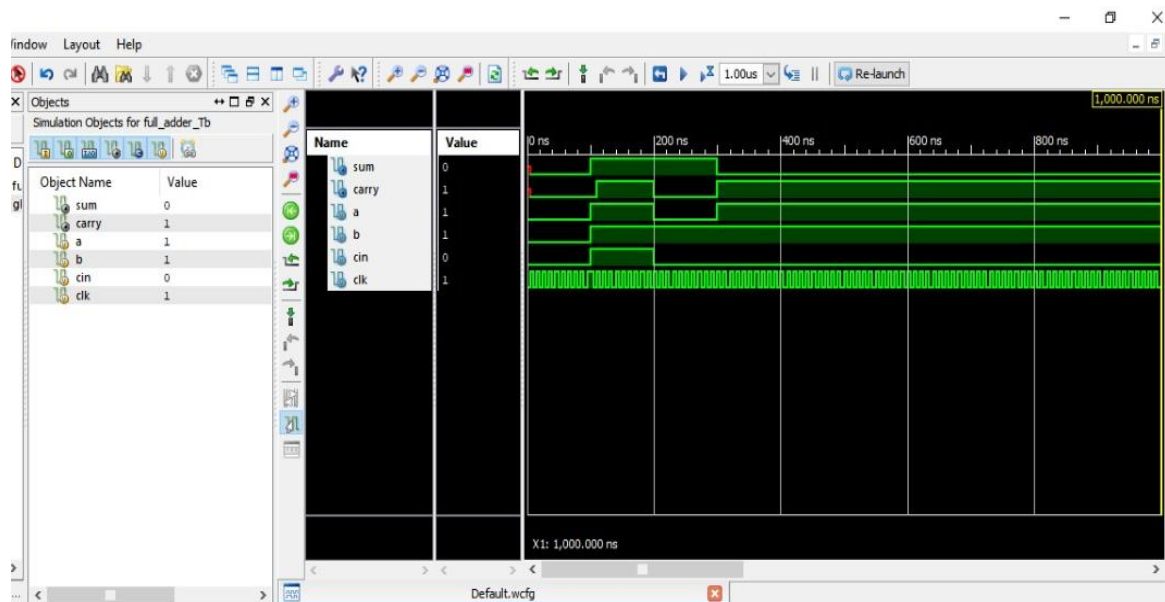

Reflection :

1. Each stage is implemented using a generate block to create multiple instances of the logic for each bit position.
2. This pipeline implementation of a half adder in Verilog demonstrates how the addition operation can be divided into stages to increase throughput and efficiency.

Booth Multiplier

CODE:

```
module BoothMul(clk,rst,start,X,Y,valid,Z);
```

```
input clk;  
input rst;  
input start;  
input signed [3:0]X,Y;  
output signed [7:0]Z;  
output valid;
```

```
reg signed [7:0] Z,next_Z,Z_temp;  
reg next_state, pres_state;  
reg [1:0] temp,next_temp;  
reg [1:0] count,next_count;  
reg valid, next_valid;
```

```
parameter IDLE = 1'b0;  
parameter START = 1'b1;
```

```
always @ (posedge clk or negedge rst)
```

```
begin
```

```
if(!rst)
```

```
begin
```

```
    Z      <= 8'd0;
```

```
    valid   <= 1'b0;
```

```
    pres_state <= 1'b0;
```

```
    temp     <= 2'd0;
```

```
    count    <= 2'd0;
```

```
end
```

```
else
```

```
begin
```

```
    Z      <= next_Z;
```

```
    valid   <= next_valid;
```

```
    pres_state <= next_state;
```

```
    temp     <= next_temp;
```

```
    count    <= next_count;
```

```
end
```

```
always @ (*)
```

```

begin
case(pres_state)
IDLE:
begin
next_count = 2'b0;
next_valid = 1'b0;
if(start)
begin
    next_state = START;
    next_temp = {X[0],1'b0};
    next_Z    = {4'd0,X};
end
else
begin
    next_state = pres_state;
    next_temp = 2'd0;
    next_Z    = 8'd0;
end
end

START:
begin
    case(temp)
        2'b10: Z_temp = {Z[7:4]-Y,Z[3:0]};
        2'b01: Z_temp = {Z[7:4]+Y,Z[3:0]};
        default: Z_temp = {Z[7:4],Z[3:0]};
    endcase
next_temp = {X[count+1],X[count]};
next_count = count + 1'b1;
next_Z    = Z_temp >>> 1;
next_valid = (&count) ? 1'b1 : 1'b0;
next_state = (&count) ? IDLE : pres_state;
end
endcase
end
endmodule

```

Test bench:

```

module booth_tb;

reg clk,rst,start;
reg signed [3:0]X,Y;
wire signed [7:0]Z;
wire valid;

```

```
always #5 clk = ~clk;
```

```
BoothMul inst (clk,rst,start,X,Y,valid,Z);
```

```
initial
```

```
$monitor($time,"X=%d, Y=%d, valid=%d, Z=%d ",X,Y,valid,Z);
```

```
initial
```

```
begin
```

```
X=5;Y=7;clk=1'b1;rst=1'b0;start=1'b0;
```

```
#10 rst = 1'b1;
```

```
#10 start = 1'b1;
```

```
#10 start = 1'b0;
```

```
@valid
```


```
#10 X=-4;Y=6;start = 1'b1;
```

```
#10 start = 1'b0;
```

```
end
```

```
endmodule
```

Output:

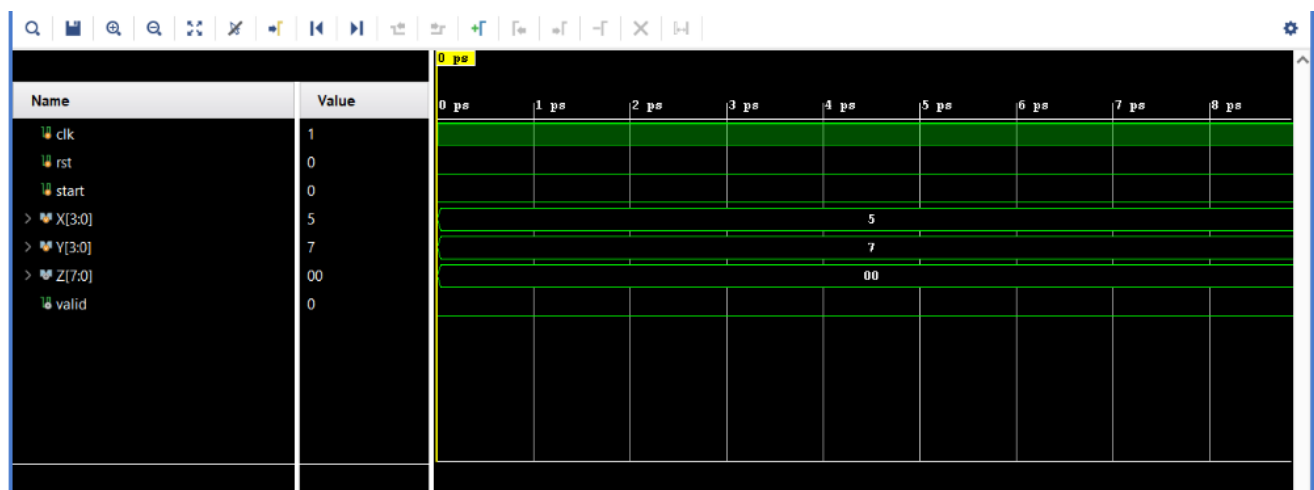

Reflection :

1. Booth Multipliers offer significant improvements in efficiency compared to traditional multiplication algorithms, particularly in hardware implementations.
2. Booth Multipliers handle signed multiplication efficiently by encoding signed numbers in a way that simplifies the multiplication process.

3. Booth Multipliers handle signed multiplication efficiently by encoding signed numbers in a way that simplifies the multiplication process

Greatest Common Divisor (GCD)

Code:

```
module GCD(out,done,clk,rst,in1,in2,go);

input [31:0]in1,in2;

input clk,rst,go;

output [31:0]out;

output done;

wire a_gt_b,a_lt_b,a_eq_b;

wire a_ld,b_ld,a_sel,b_sel;

wire output_en;

controller c1(a_ld,b_ld,a_sel,b_sel,output_en,done,clk,rst,go,a_gt_b,a_lt_b,a_eq_b);

datapath d1(a_gt_b,a_lt_b,a_eq_b,out,output_en,clk,rst,a_ld,b_ld,a_sel,b_sel,in1,in2);

endmodule
```

Test bench:

```
module testbench_GCD;

    reg clk;

    reg rst;

    reg [31:0] in1;
```

```

    reg [31:0] in2;

    reg go;

wire [31:0] out;

    wire done;


//integer i;

    initial clk=0;

    always@(clk) #20 clk <= ~clk;

    GCD uut (

        .out(out),

        .done(done),

        .clk(clk),

        .rst(rst),

        .in1(in1),

        .in2(in2),

        .go(go));

task initialize;

    begin

        in1=0;

        in2=0;

        go=0;

    end

endtask

```



```

task reset;

begin

    @(negedge clk)

        rst <=1;

        go<=0;

        @(negedge clk)

            rst <=0;

            go <=1;

        end endtask

task calculate(input [31:0]a,input [31:0]b);

begin

    @(negedge clk)

        go<=1;

        in1 <= a;

            in2 <= b;

            #50 go<=0;

            #10000;

        end

    endtask

initial begin

    $monitor($time," %d %d %d",in1,in2,out);

    reset;

    initialize;

```


Reflection

1. Calculating the GCD involves finding the largest integer that divides both numbers without leaving a remainder.
2. GCD computations have practical applications in computer science, such as in cryptography, where it is used in key generation and other cryptographic protocols.

FIR

Code

```
module FIR(F_out, F_in, clk);  
  
    input signed [15:0]F_in;  
  
    input clk;  
  
    output reg signed [31:0]F_out;  
  
    reg signed [15:0]b[0:9];  
  
    reg signed [15:0]shift[0:9];  
  
    initial  
  
    begin  
  
        b[0]<=16'd1;  
  
        b[1]<=16'd1;  
  
        b[2]<=16'd1;  
  
        b[3]<=16'd1;  
  
        b[4]<=16'd1;
```

b[5]<=16'd1;

b[6]<=16'd1;

b[7]<=16'd1;

b[8]<=16'd1;

b[9]<=16'd1;

end

always@(posedge clk)

begin

shift[0]<=F_in;

shift[1]<=shift[0];

shift[2]<=shift[1];

shift[3]<=shift[2];

shift[4]<=shift[3];

shift[5]<=shift[4];

shift[6]<=shift[5];

shift[7]<=shift[6];

shift[8]<=shift[7];

shift[9]<=shift[8];

end

always@(posedge clk)

begin

F_out<=((shift[0]*b[0])+(shift[1]*b[1])+(shift[2]*b[2])+


(shift[3]*b[3])+(shift[4]*b[4])+(shift[5]*b[5])+

```
(shift[6]*b[6])+(shift[7]*b[7])+(shift[8]*b[8])+(shift[9]*b[9]));
```

```
end
```

```
endmodule
```

Output

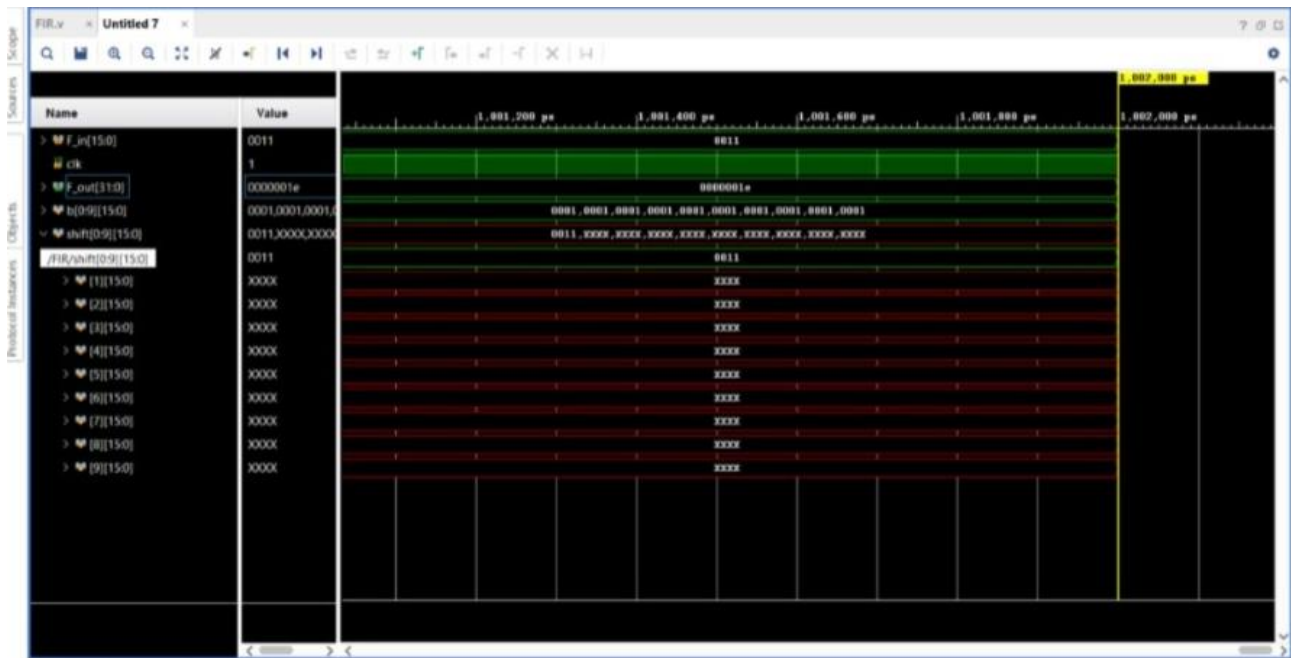

Reflection

1. understood of how FIR filters operate by using a simple 3-tap filter. Each new input sample is multiplied by a coefficient and summed with the previous samples' results.
2. The use of shift registers to store previous input samples is crucial in FIR filter design. This example demonstrates the use of a shift register to implement the delay elements needed for FIR filtering

Traffic Light

Code:

```
module cyclic_lamp (clk, light);

    input clk;

    output reg [2:0] light; // Light output should be 3 bits for RED, GREEN, YELLOW

    parameter s0 = 0; // Initial state

    parameter s1 = 1;

    parameter s2 = 2;

    parameter RED = 3'b100;

    parameter GREEN = 3'b010;

    parameter YELLOW = 3'b001;

    reg [1:0] state = s0; // Initialize state to s0

    always @(posedge clk) begin

        case (state)

            s0: begin

                light <= GREEN;

                state <= s1;

            end

            s1: begin

                light <= YELLOW;

                state <= s2;

            end

        end

    end
```

```

s2: begin

    light <= RED;

    state <= s0;

end

default: begin // Explicitly handle undefined states

    light <= RED; // Set light to RED for safety

    state <= s0; // Transition to initial state

end


endcase



end

endmodule

```

Output:

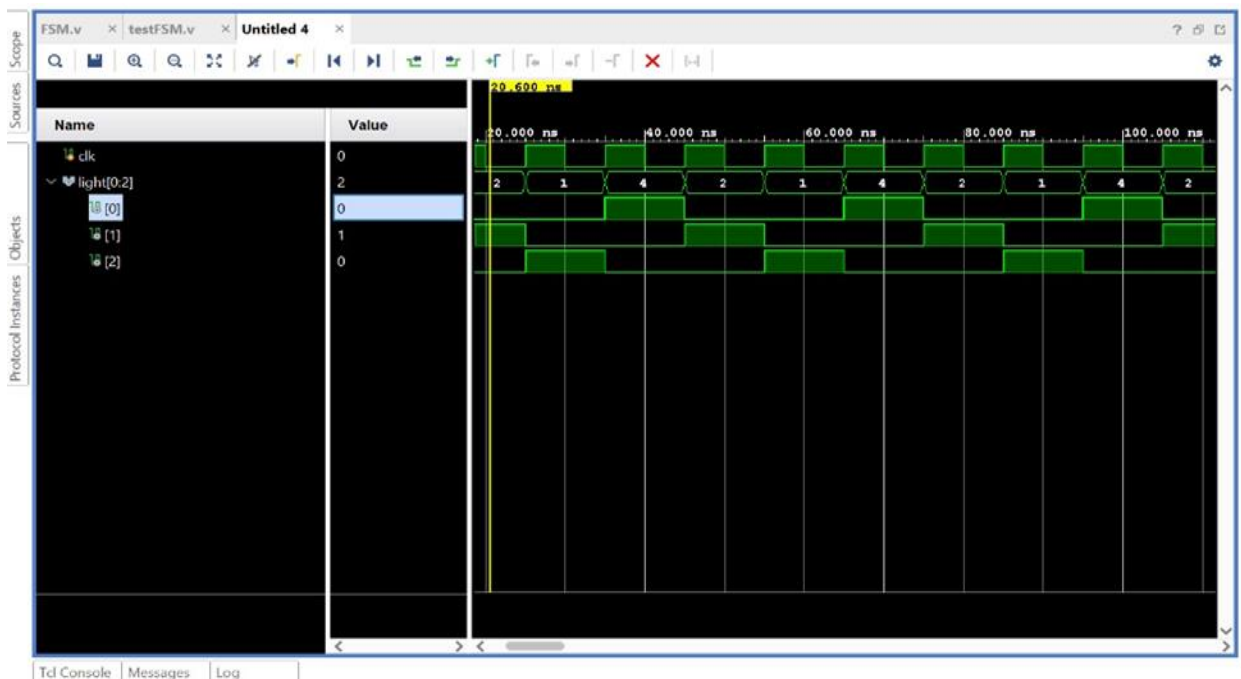

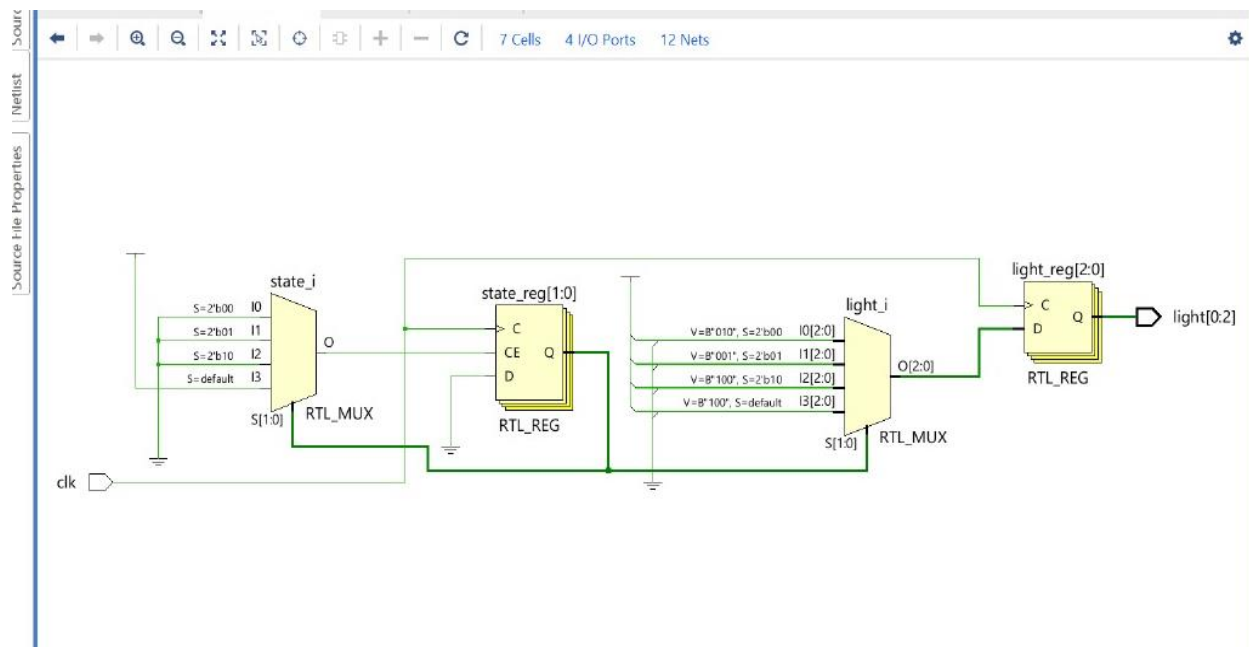 

Design and implement a pipeline that carries the following stage wise operations.

Code:

```
module pipeline (  
input wire clk,  
input wire rst,  
input wire [3:0] rs1, rs2, rd, rp, // Register addresses  
input wire [2:0] alu_fun, // ALU function code  
input wire [15:0] mem_addr, // Memory address  
output reg [15:0] mem_data_out // Data output to memory  
);  
  
// Register file  
reg [15:0] reg_file [0:15];  
  
// ALU  
reg [15:0] a, b, z;  
  
// Memory  
reg [15:0] memory [0:255];  
  
// ALU function definitions localparam ALU_ADD = 3'b000,  
ALU_SUB = 3'b001,  
ALU_AND = 3'b010,  
ALU_OR = 3'b011,  
ALU_XOR = 3'b100,  
ALU_NOT = 3'b101;  
  
// Pipeline stages  
always @(posedge clk or posedgerst) begin  
if (rst) begin  
a <= 16'd0;  
b <= 16'd0;  
z <= 16'd0;  
mem_data_out <= 16'd0;  
end else begin  
// Stage 1: Read from register file
```

```

a <= reg_file[rs1];
b <= reg_file[rs2];

// Stage 2: Perform ALU operation
case (alu_fun)
  ALU_ADD: z <= a + b;
  ALU_SUB: z <= a - b;
  ALU_AND: z <= a & b;
  ALU_OR: z <= a | b;
  ALU_XOR: z <= a ^ b;
  ALU_NOT: z <= ~a;
  default: z <= 16'd0;
endcase

// Stage 3: Write to register file
reg_file[rd] <= z;

// Stage 4: Write to memory memory
[mem_addr] <= z;
mem_data_out <=
  z; end
end endmodule

```

Test bench:

```

module pipeline_tb;
reg clk;
reg rst;
reg [3:0] rs1, rs2, rd, rp; // Register addresses reg [2:0] alu_fun;
// ALU function code reg [15:0] mem_addr; // Memory address
wire [15:0] mem_data_out; // Data output to memory

// Instantiate the pipeline module pipeline uut (
.clk(clk),
.rst(rst),
.rs1(rs1),
.rs2(rs2),
.rd(rd),
.rp(rp),

```

```

.alu_fun(alu_fun),
.mem_addr(mem_addr),
.mem_data_out(mem_data_out)
);

// Clock generation
always #5 clk = ~clk;

initial begin
// Initialize signals
clk = 0;
rst = 1;
rs1 = 4'd0;
rs2 = 4'd1;
rd = 4'd2;
rp = 4'd3;
alu_fun = 3'd0;
mem_addr = 16'd0;

// Initialize register file and memory
uut.reg_file[0] = 16'd10; // Register 0
uut.reg_file[1] = 16'd20; // Register 1
uut.reg_file[2] = 16'd0; // Register 2
uut.reg_file[3] = 16'd0; // Register 3

#10 rst = 0; // Release reset

// Test case 1: ADD rs1 and rs2, store in rd and memory
alu_fun = 3'b000; // ADD operation
rs1 = 4'd0;
rs2 = 4'd1;
rd = 4'd2;
mem_addr = 16'd0;
#10;

// Check results
$display("Test Case 1: ADD");
$display("reg_file[2] = %d, memory[0] = %d", uut.reg_file[2], uut.memory[0]);
$display("mem_data_out = %d", mem_data_out);
// Test case 2: SUB rs1 and rs2, store in rd and memory

```

```

alu_fun = 3'b001; // SUB operation
rs1 = 4'd0;
rs2 = 4'd1;
rd = 4'd2;
mem_addr = 16'd1;
#10;

// Check results
$display("Test Case 2: SUB");
$display("reg_file[2] = %d, memory[1] = %d", uut.reg_file[2], uut.memory[1]);
$display("mem_data_out = %d", mem_data_out);

// Test case 3: AND rs1 and rs2, store in rd and memory
alu_fun = 3'b010; // AND operation
rs1 = 4'd0;
rs2 = 4'd1;
rd = 4'd2;
mem_addr = 16'd2;
#10;

// Check results
$display("Test Case 3: AND");
$display("reg_file[2] = %d, memory[2] = %d", uut.reg_file[2], uut.memory[2]);
$display("mem_data_out = %d", mem_data_out);

// Test case 4: OR rs1 and rs2, store in rd and memory
alu_fun = 3'b011; // OR operation
rs1 = 4'd0;
rs2 = 4'd1;
rd = 4'd2;
mem_addr = 16'd3;
#10;
// Check results
$display("Test Case 4: OR");
$display("reg_file[2] = %d, memory[3] = %d", uut.reg_file[2], uut.memory[3]);
$display("mem_data_out = %d", mem_data_out);

// Test case 5: XOR rs1 and rs2, store in rd and memory
alu_fun = 3'b100; // XOR operation
rs1 = 4'd0;


```

```


    rs2 = 4'd1;
    rd = 4'd2;
    mem_addr = 16'd4;
    #10;
    // Check results
    $display("Test Case 5: XOR");
    $display("reg_file[2] = %d, memory[4] = %d", uut.reg_file[2], uut.memory[4]);
    $display("mem_data_out = %d", mem_data_out);
    // Test case 6: NOT rs1, store in rd and memory
    alu_fun = 3'b101; // NOT operation
    rs1 = 4'd0;
    rs2 = 4'd0; // rs2 is irrelevant for NOT operation
    rd = 4'd2;
    mem_addr = 16'd5;
    #10;
    $display("Test Case 6: NOT");
    $display("reg_file[2] = %d, memory[5] = %d", uut.reg_file[2], uut.memory[5]);
    $display("mem_data_out = %d", mem_data_out);
    $stop;
end
endmodule

```

OUTPUT:

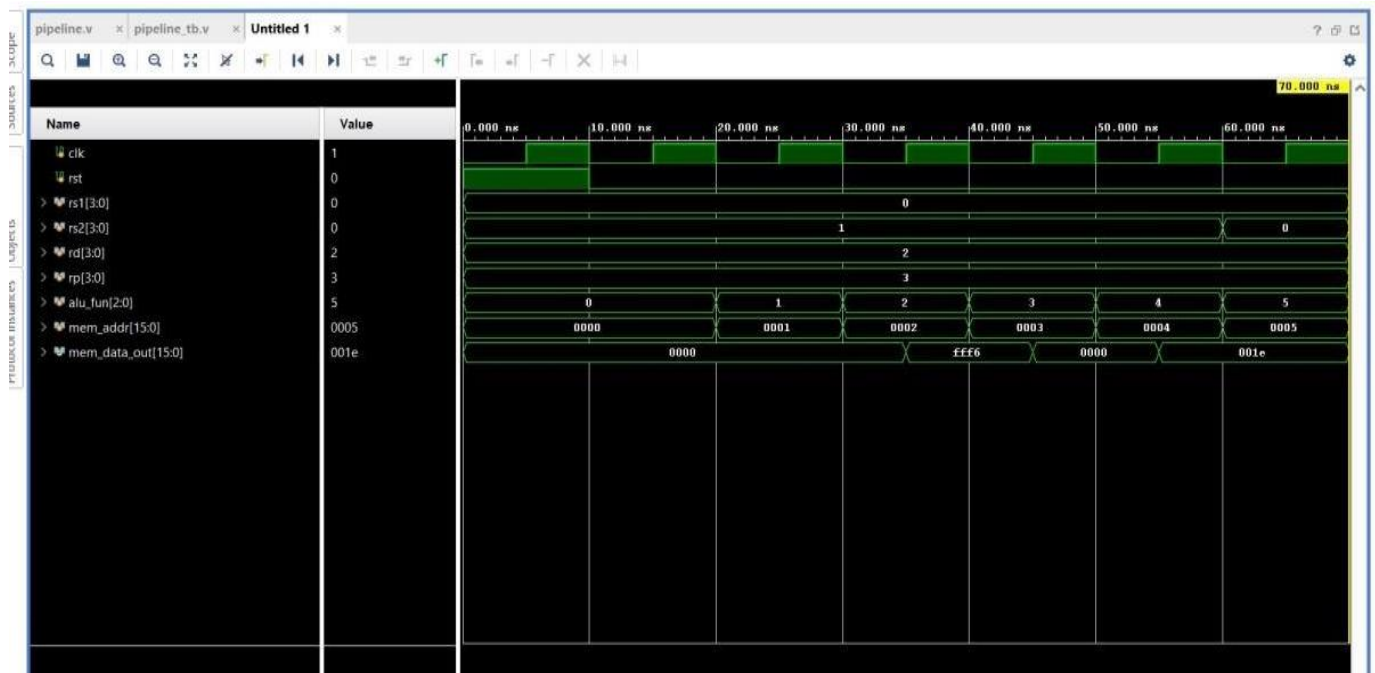

Schematic

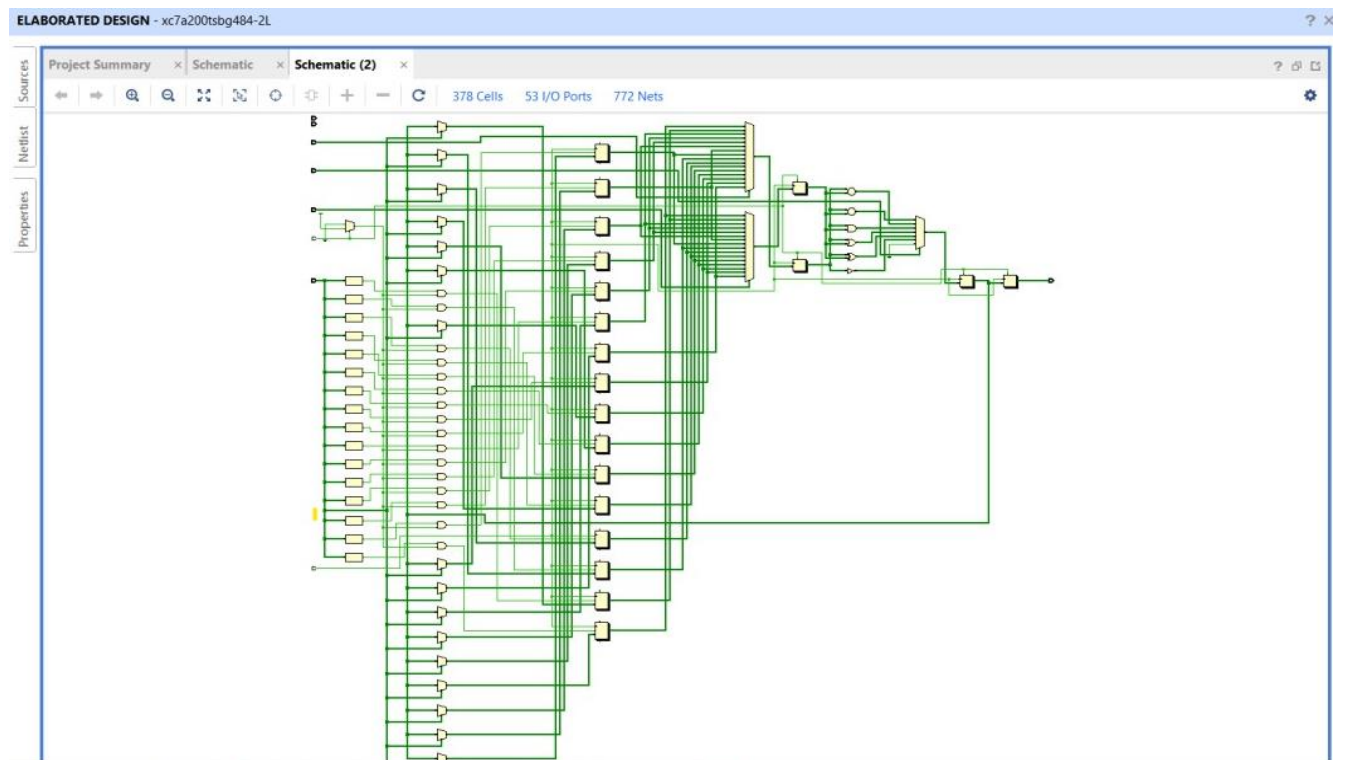

Reflections :

1. understanding of pipeline design, specifically how data flows through multiple stages (fetch, decode, execute, memory access, write-back). This is essential for optimizing CPU performance and increasing instruction throughput
2. The implementation of a reset mechanism to initialize pipeline stages and other components is a critical aspect of designing robust digital systems.

NON PIPELINE

Code:

```
module npipe (F, A, B, C, D, clk);
parameter n = 10;
input [n-1:0] A, B, C, D;
input
clk;
output reg [n-1:0] F;
  reg [n-1:0] x1, x2, x3, d;
always @(posedge clk)
begin

// Perform all operations in one clock cycle
//blocking assignment
x1 = A + B;
x2 = C - D;
//d = D;
x3 = x1 + x2;

F = x3 * D;
end
endmodule
```

Testbench:


```

`timescale 1ns/1ps
module npipe_test;
// Parameters
parameter n = 10;

// Inputs
reg [n-1:0] A, B, C, D;
reg clk;
//
Outputs wire[
n-1:0] F;

// Instantiate the Unit Under Test (UUT)
npipe #(n) uut (
.A(A),
.B(B),
.C(C),
.D(D),
.clk(clk),
.F(F)
);

initial begin
// Initialize Inputs
clk = 0;
A = 0; B = 0; C = 0; D = 0;

#5 A = 10; B = 12; C = 6; D = 3; // Expected F = (10+12 + 6-3) * 3 = 75
#10 A = 10; B = 10; C = 5; D = 3; // Expected F = (10+10 + 5-3) * 3 = 66
#10 A = 20; B = 11; C = 1; D = 4; // Expected F = (20+11 + 1-4) * 4 = 112
#10 A = 15; B = 10; C = 8; D = 2; // Expected F = (15+10 + 8-2) * 2 = 62
#10 A = 8; B = 15; C = 5; D = 0; // Expected F = (8+15 + 5-0) * 0 = 0
#10 A = 10; B = 20; C = 5; D = 3; // Expected F = (10+20 + 5-3) * 3 = 96
#10 A = 10; B = 10; C = 30; D = 1; // Expected F = (10+10 + 30-1) * 1 = 49
#10 A = 30; B = 1; C = 2; D = 4; // Expected F = (30+1 + 2-4) * 4 = 116

// Finish simulation
#40 $finish;
end

```


```


// Clock generation
always begin
    #5 clk = ~clk; // Toggle clock every 5 time units end

initial begin
    // Monitor changes
    $dumpfile("npipe.vcd");
    $dumpvars(0, npipe_test);
    $monitor("Time: %3d, A = %d, B = %d, C = %d, D = %d, F = %d", $time, A, B, C, D, F);end
Endmodule

```

OUTPUT

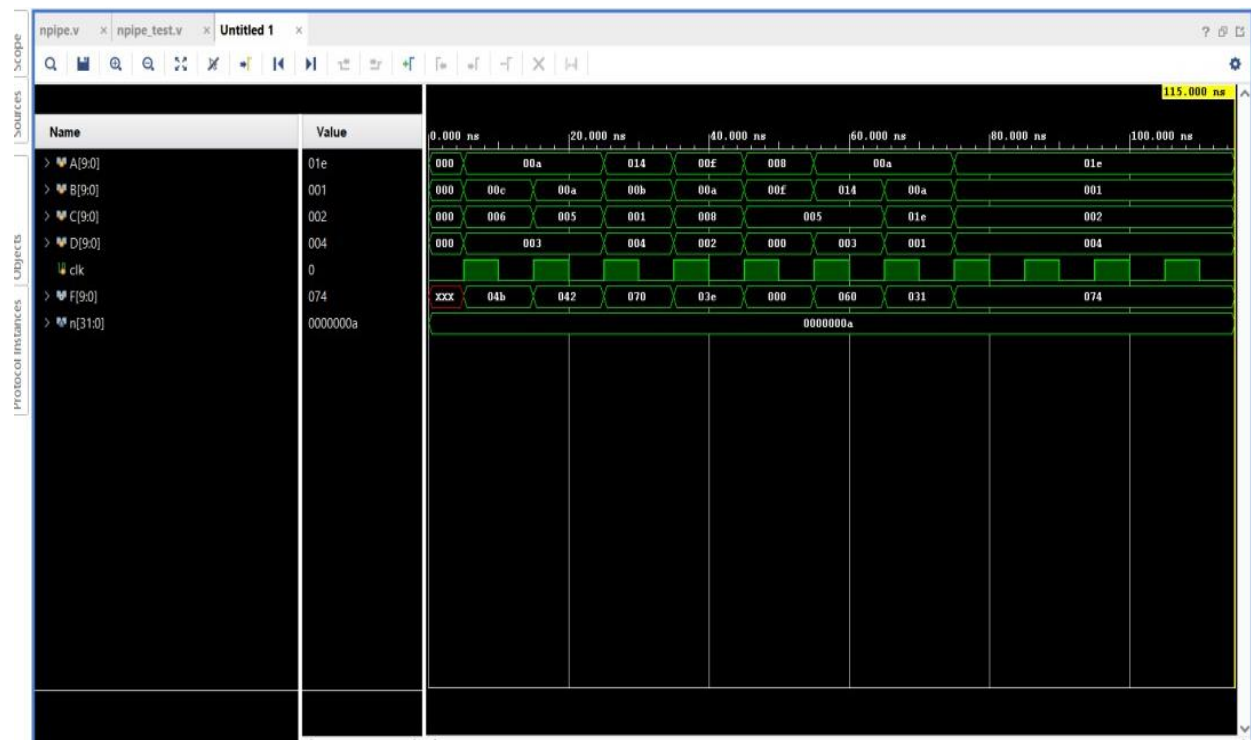

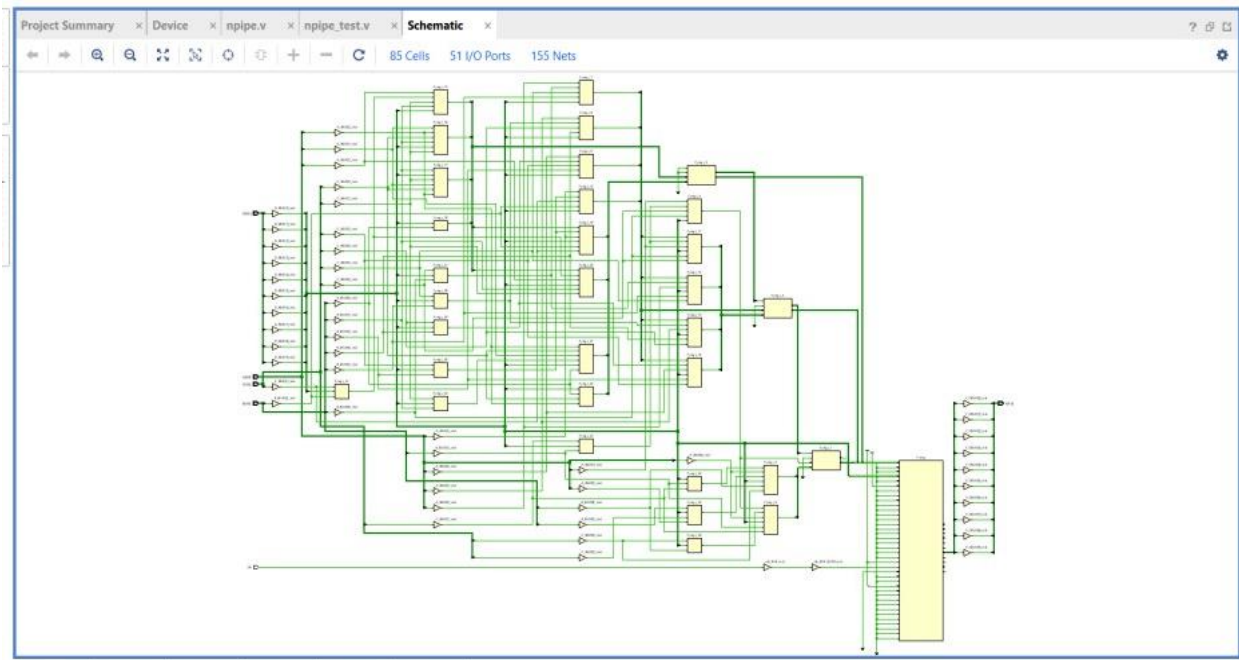

Reflections :

1. Calculating the data path delays from console window
2. Calculating LUT values and comparing with pipelined logic
3. does not implement a true multi-stage pipeline, but the testbench simulates the behavior of a single-stage pipeline where all operations are completed within one clock cycle. This provides a basic understanding of how pipelines can be simulated and verified

Sequence detector

Code


```
module detector(  
    input x,  
    input clk,  
    input reset,  
    output reg z  
);  
parameter s0=0,s1=1,s2=2,s3=3;  
reg[0:1]Ps,Ns;  
always@(posedge clk or posedge reset)  
if(reset)  
    Ps<=s0;  
else  
    Ps<=Ns;  
always@(Ps,x)  
case(Ps)  
s0:begin  
    z= x? 0:0;  
    Ns= x? s0:s1;  
end  
s1:begin  
    z= x? 0:0;  
    Ns = x? s2:s1;  
end  
s2:begin  
    z= x ? 0: 0;  
    Ns = x? s3:s1;  
end  
s3:begin  
    z= x? 0:1;  
    Ns = x? s0:s1;  
end
```

```
endcase  
Endmodule
```


Test bench

```
module seq_tb;  
reg clk,x,reset;  
wire z;  
detector SEQ(x,clk,reset,z);  
initial  
begin  
$dumpfile("sequence.vcd");  
$dumpvars(0,seq_tb);  
clk=1'b0;  
reset =1'b1;  
#15 reset = 1'b0;  
end  
always #5 clk = ~clk;  
initial  
begin  
#12 x=0;#10 x=0;#10 x=1; #10 x=1;  
#10 x=0;#10 x=1;#10 x=1; #10 x=0;  
#12 x=0;#10 x=1;#10 x=1; #10 x=0;  
#10 $finish;  
end  
endmodule
```

Output

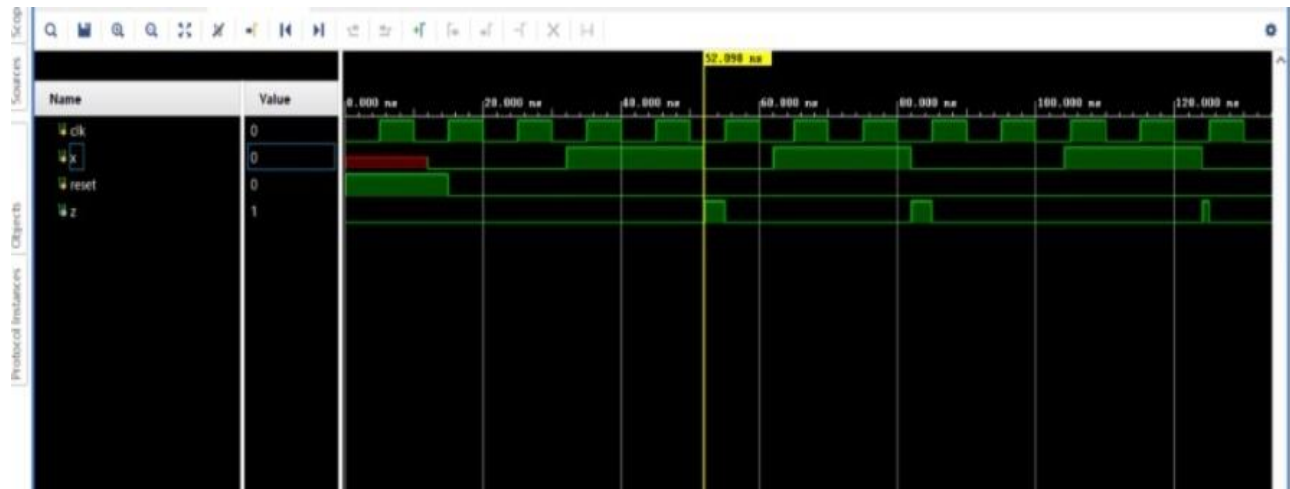

Schematic

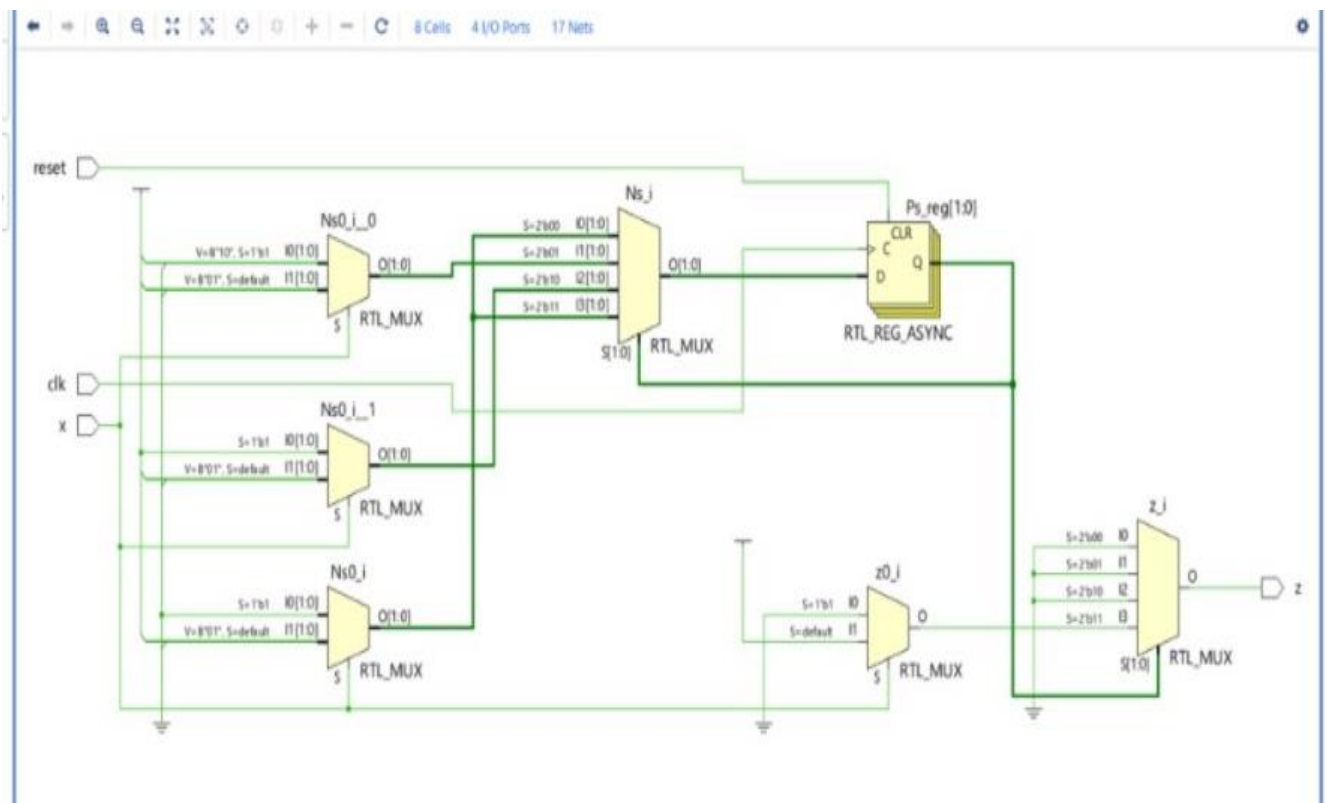

Reflection

1. implementing FSMs for sequence detection. FSMs are a fundamental concept in digital design and are widely used in various applications
2. The sequence detector essentially performs edge detection by checking the current state and input to determine the next state and output. This principle is useful in many digital design scenarios, such as debouncing switches and serial data communication

Design port RAM of 100MB capacity Implementation of functions(FA) using ROM.

Code

```
module dual_port_ram(  
input [7:0] data_a, data_b, //input data  
  
input [5:0] addr_a, addr_b, //Port A and Port B address  
input we_a, we_b, //write enable for Port A and Port B  
input clk, //clk  
output reg [7:0] q_a, q_b //output data at Port A and Port B  
);  
  
reg [7:0] ram [63:0]; //8*64 bit ram  
  
always @ (posedgeclk)  
begin  
if(we_a)  
    ram[addr_a] <= data_a;  
else  
    q_a<= ram[addr_a];  
end
```

```

always @ (posedgeclk)
begin
    if(we_b)
        ram[addr_b] <= data_b; else
        q_b<= ram[addr_b];
    end
endmodule

```

Testbench

```

module dual_port_ram_tb;
    reg [7:0] data_a, data_b; //input data
    reg [5:0] addr_a, addr_b; //Port A and Port B address
    reg we_a, we_b; //write enable for Port A and Port B
    reg clk; //clk
    wire [7:0] q_a, q_b; //output data at Port A and Port B

    dual_port_ram dpr1(
        .data_a(data_a),
        .data_b(data_b),
        .addr_a(addr_a),
        .addr_b(addr_b),
        .we_a(we_a),
        .we_b(we_b),
        .clk(clk),
        .q_a(q_a),
        .q_b(q_b)
    );

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1, dual_port_ram_tb);

        clk=1'b1;
        forever #5 clk = ~clk;
    end

```



```
initial begin
data_a = 8'h33;
addr_a = 6'h01;

data_b = 8'h44;
addr_b = 6'h02;

we_a = 1'b1;
we_b = 1'b1;

#10;

data_a = 8'h55;
addr_a = 6'h03;

addr_b = 6'h01;
we_b = 1'b0;
#10;


addr_a = 6'h02;
addr_b = 6'h03;
we_a = 1'b0;
#10;

addr_a = 6'h01;


data_b = 8'h77;
addr_b = 6'h02;
we_b = 1'b1; #10;
end

initial
#40 $stop;
Endmodule
```

Output

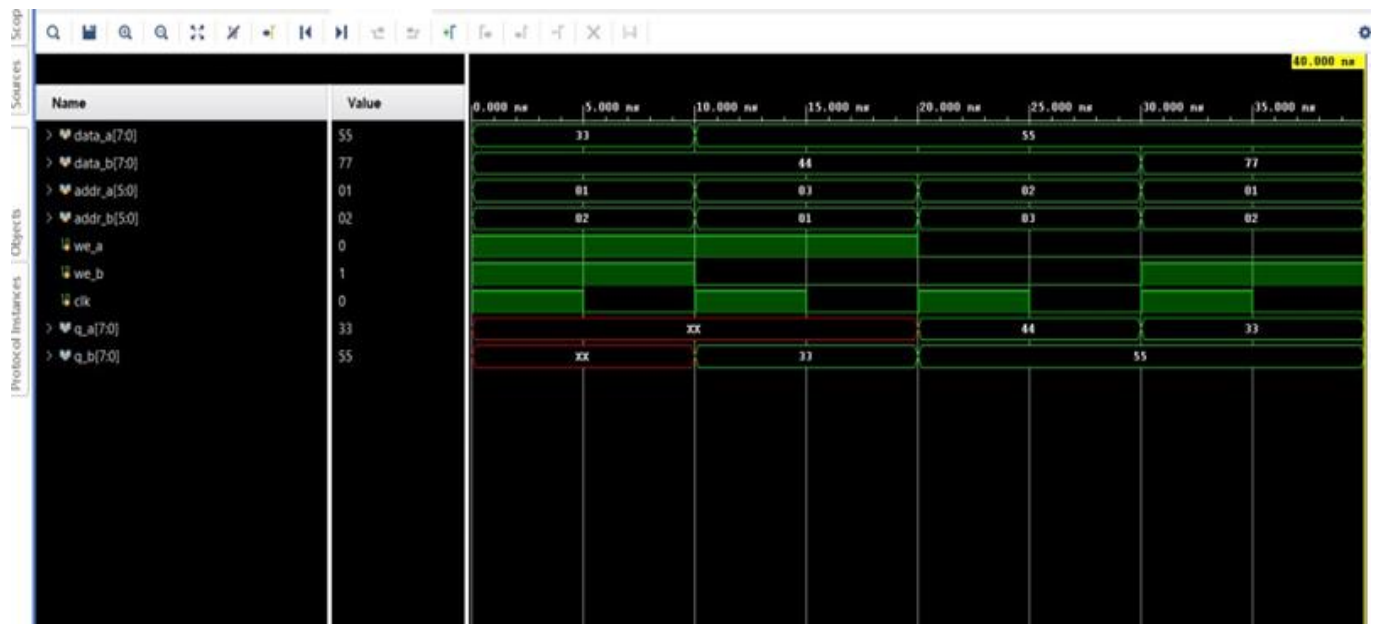

Schematic:

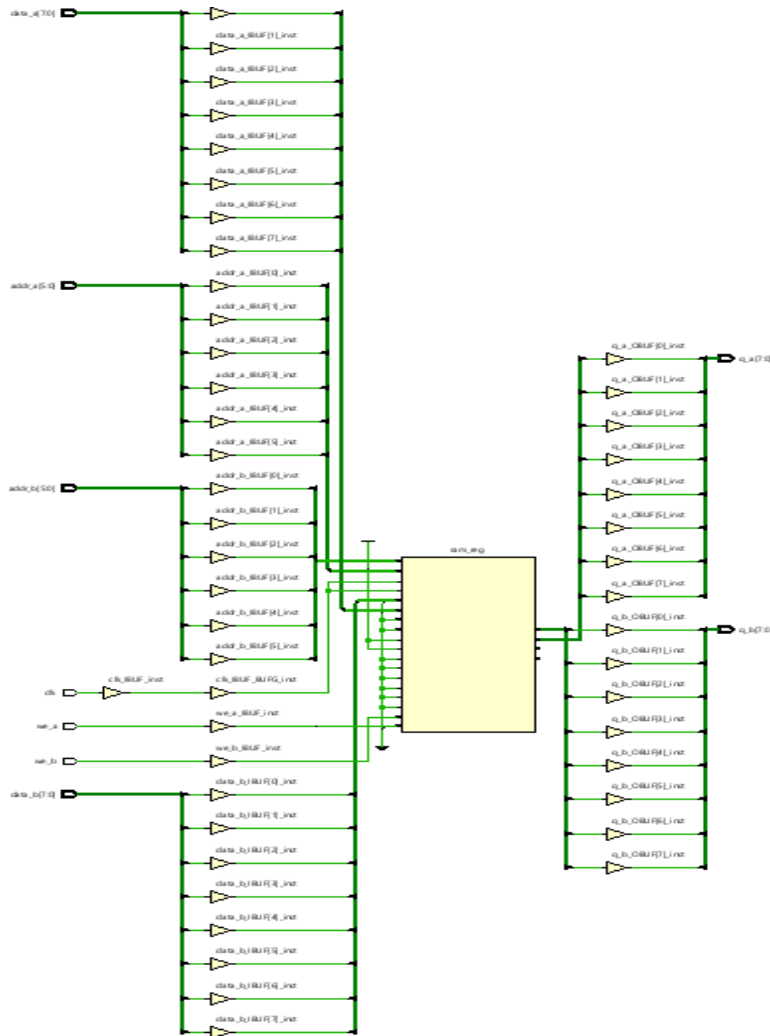

Reflection:

1. Dual-port RAM allows simultaneous read/write access to different addresses, which is critical for high-performance systems where multiple data operations need to be conducted concurrently.
2. ROM-Based Function Implementation.

3 Stage ALU

Code

```
module ALU_16bit_3s_Pipelined(  
    input clk,           // Clock signal  
    input reset,         // Reset signal  
    input [15:0] a,       // First operand  
    input [15:0] b,       // Second operand  
    input [2:0] sel,      // Operation selector  
    output reg [15:0] y,   // Result of the operation  
    output reg cout,      // Carry out for addition  
    output reg zero       // Zero flag  
);  
  
// Pipeline registers  
reg [15:0] a_reg1, b_reg1;  
reg [2:0] sel_reg1;  
reg [16:0] result_reg2;  
reg [15:0] y_reg3;  
reg cout_reg3, zero_reg3;  
  
// Fetch/Decode Stage  
always @(posedge clk or posedge reset) begin  
    if (reset) begin  
        a_reg1 <= 16'b0;  
        b_reg1 <= 16'b0;  
        sel_reg1 <= 3'b0;  
    end else begin  
        a_reg1 <= a;  
        b_reg1 <= b;  
        sel_reg1 <= sel;  
    end  
end  
  
// Execute Stage  
always @(posedge clk or posedge reset) begin  
    if (reset) begin
```

```

    result_reg2 <= 17'b0;
end else begin
    case (sel_reg1)
        3'b000: begin // Addition
            result_reg2 <= a_reg1 + b_reg1;
        end
        3'b001: begin // Subtraction
            result_reg2 <= a_reg1 - b_reg1;
        end
        3'b010: begin // AND
            result_reg2 <= {1'b0, a_reg1 & b_reg1};
        end
        3'b011: begin // OR
            result_reg2 <= {1'b0, a_reg1 | b_reg1};
        end
        3'b100: begin // XOR
            result_reg2 <= {1'b0, a_reg1 ^ b_reg1};
        end
        3'b101: begin // Left Shift
            result_reg2 <= {1'b0, a_reg1 << 2};
        end
        3'b110: begin // Right Shift
            result_reg2 <= {1'b0, a_reg1 >> 2};
        end
        default: begin // Default to zero
            result_reg2 <= 17'b0;
        end
    endcase
end
end

// Write Back Stage
always @(posedge clk or posedge reset) begin
    if (reset) begin
        y_reg3 <= 16'b0;
        cout_reg3 <= 1'b0;
        zero_reg3 <= 1'b0;
    end else begin
        y_reg3 <= result_reg2[15:0];
        cout_reg3 <= result_reg2[16];
    end
end

```

```

        zero_reg3 <= (result_reg2[15:0] == 16'b0);
    end
end

// Output assignments
always @(*) begin
    y = y_reg3;
    cout = cout_reg3;
    zero = zero_reg3;
end

endmodule

```

Testbench

```

module ALU_16bit_3s_Pipelined_TB;

    reg clk;          // Clock signal
    reg reset;        // Reset signal
    reg [15:0] a;      // First operand
    reg [15:0] b;      // Second operand
    reg [2:0] sel;     // Operation selector
    wire [15:0] y;     // Result of the operation
    wire cout;         // Carry out for addition
    wire zero;         // Zero flag

    // Instantiate the ALU
    ALU_16bit_3s_Pipelined uut (
        .clk(clk),
        .reset(reset),
        .a(a),
        .b(b),
        .sel(sel),
        .y(y),
        .cout(cout),
        .zero(zero)
    );

    // Clock generation

```

```
always begin
    #5 clk = ~clk;
end
```

```
initial begin
```

```
    // Initialize signals
```

```
    clk = 0;
```

```
    reset = 1;
```

```
    a = 0;
```

```
    b = 0;
```

```
    sel = 0;
```

```
    #10;
```

```
    reset = 0;
```

```
    // Monitor the signals
```

```
    $monitor('Time = %d: a = %b, b = %b, sel = %b, y = %b, cout = %b, zero = %b',
$time, a, b, sel, y, cout, zero);
```

```
    // Test addition
```

```
    a = 16'b00000000000001111; b = 16'b00000000000000001; sel = 3'b000;
```

```
    #20;
```

```
    // Test subtraction
```

```
    a = 16'b00000000000001111; b = 16'b00000000000000001; sel = 3'b001;
```

```
    #20;
```

```
    // Test AND
```

```
    a = 16'b00000000000001111; b = 16'b00000000000000101; sel = 3'b010;
```

```
    #20;
```

```
    // Test OR
```

```
    a = 16'b00000000000001111; b = 16'b00000000000000101; sel = 3'b011;
```

```
    #20;
```

```
    // Test XOR
```

```
    a = 16'b00000000000001111; b = 16'b00000000000000101; sel = 3'b100;
```

```
    #20;
```

```
    // Test Left Shift
```

```
    a = 16'b00000000000001111; b = 16'b00000000000000000; sel = 3'b101;
```

```

#20;

// Test Right Shift
a = 16'b00000000000001111; b = 16'b00000000000000000; sel = 3'b110;
#20;


// Test Zero Flag
a = 16'b00000000000000000; b = 16'b00000000000000000; sel = 3'b000;
#20;

// End of simulation
$stop;
end


endmodule

```

Output

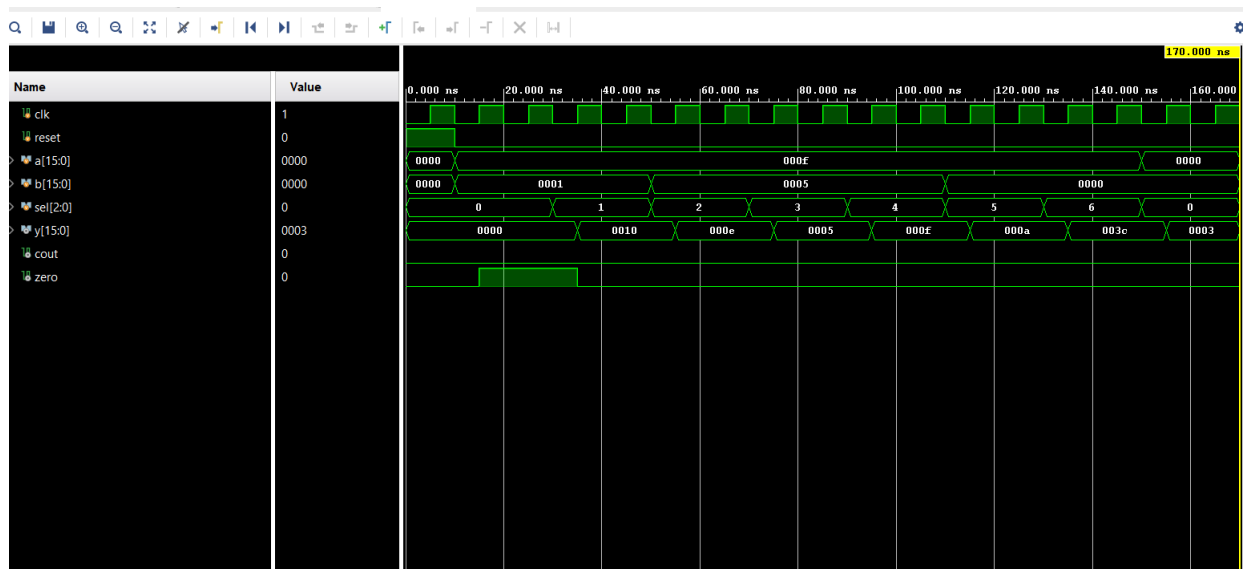

Schematic

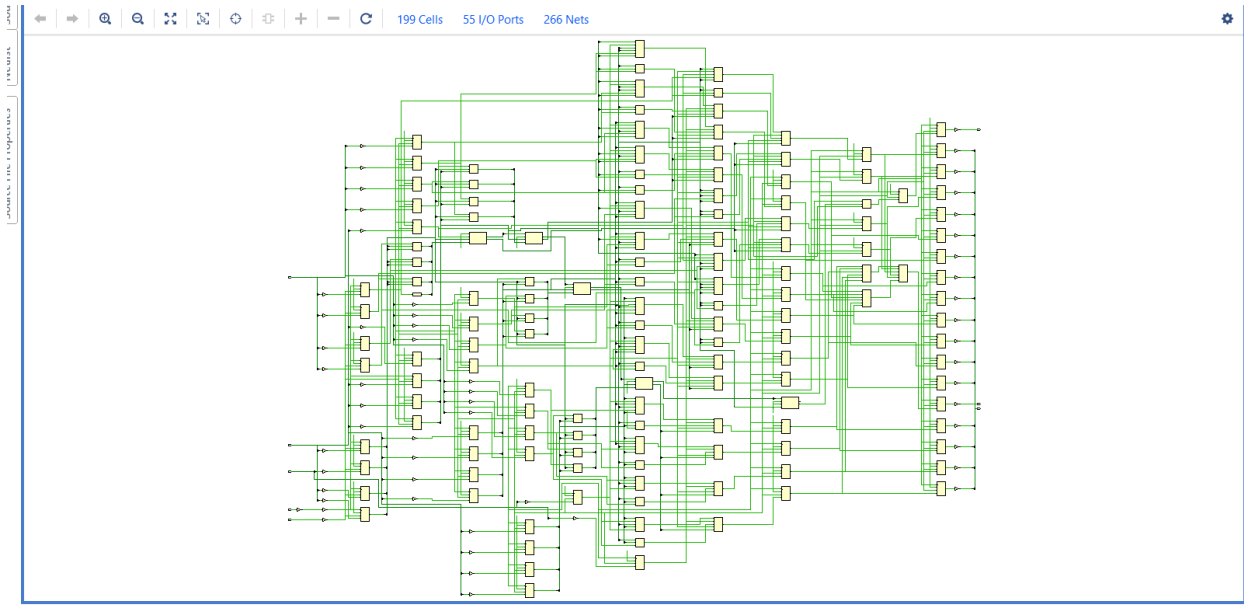

Reflection

1. Understand various arithmetic and logic operations like addition, subtraction, AND, OR, etc.
2. Learn to design a pipelined digital system with multiple stages to improve performance.
3. Gain proficiency in writing and simulating Verilog code to design and test digital systems.